

Microwave Basics



Microwave energy is transported by means of transmission lines.

TEM No longitudinal component of \vec{E} or \vec{B}
 Requires two conductors

TE, TM Present in waveguide (single conductor)



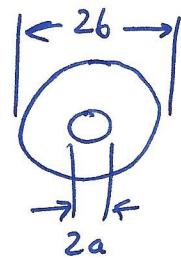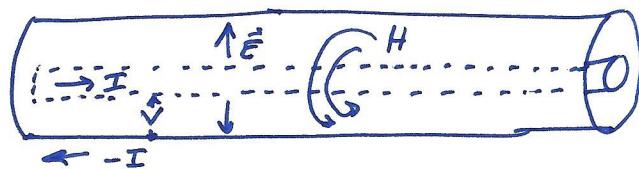Coaxial Cables are the most common form of transmission line



The radial electric field is given by

$$E = \frac{V}{\ln(b/a)} \cdot \frac{1}{r} \quad (\text{V/m})$$

The axial magnetic field is given by

$$H = \frac{I}{2\pi r} \cdot \frac{1}{r} \quad (\text{A/m})$$

Fig. 1.1-3(a) is a nice picture of the coaxial TEM mode.

2

The speed of light in the coaxial cable is

$$v_{ph} = \frac{c}{\sqrt{\epsilon_r}} = \frac{1}{\sqrt{\epsilon_0 \epsilon_r \mu_0}}$$

ϵ_r = relative permittivity

μ_r = relative permeability

$$\lambda f = v_{ph} \quad \lambda_{\text{free}} = \frac{\lambda_{\text{free}}}{\sqrt{\epsilon_r}}$$

$$V(t) = |V| e^{i(2\pi ft + \phi)}$$

$$V(x,t) = |V| e^{i(2\pi ft + \phi - \beta x)}$$

$$\beta = \frac{2\pi}{\lambda}$$

If a wave propagates a distance L , its phase advances by $\beta L = 2\pi L/\lambda$.

1.3 Characteristic Impedance

A property of a transmission line is its characteristic impedance. It is defined as the ratio of voltage to current at a given point;

$$Z_c = \left. \frac{V}{I} \right|_{\text{point}} \quad (2)$$

True for a travelling wave. The characteristic


Impedance for a standing wave is not constant, since that is a combination of two waves travelling in opposite directions. Their

$$Z_c(x) = \frac{V_{\text{TOTAL}}(x)}{I_{\text{TOTAL}}(x)}$$

varies down the line.

~~For two travelling waves;~~

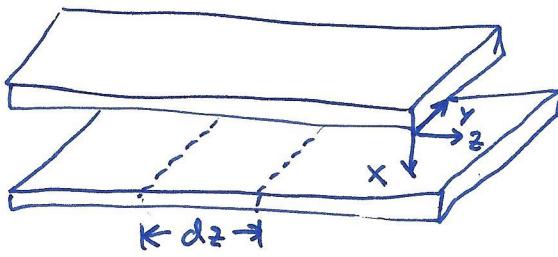Derive the equations for a travelling wave on a transmission line;



$$\begin{array}{c} I \xrightarrow{\text{L}} \\ \downarrow \quad \uparrow \\ \text{---} \end{array} \xrightarrow{\text{C}} \begin{array}{c} I + \frac{\partial I}{\partial z} dz \\ V + \frac{\partial V}{\partial z} dz \end{array}$$

$L = \text{inductance/length}$

$C = \text{capacitance/length}$

Inductance is associated with the flux produced by the oppositely directed currents in the pair of conductors. When the currents vary in time, there is a voltage change along the line.

The change in voltage is the inductance times the time rate of change of the current.

$$\text{Voltage change} = \frac{\partial V}{\partial z} dz = -(L dz) \frac{\partial I}{\partial t}$$

A change in current along the line is merely the ~~current~~ ^{voltage} that is shunted across the distributed capacitance. The rate of decrease of the current with distance is the capacitance times the time rate of change of the voltage.

$$\text{Current change} = \frac{\partial I}{\partial z} dz = - (L dz) \frac{\partial V}{\partial t}$$

So we have the two equations

$$\frac{\partial V}{\partial z} = - L \frac{\partial I}{\partial t}$$

$$\frac{\partial I}{\partial z} = - C \frac{\partial V}{\partial t}$$

By taking further partial derivatives, one can get a wave equation for either V or I ,

$$\frac{\partial^2 V}{\partial z^2} = LC \frac{\partial^2 V}{\partial t^2} = \frac{1}{V_{ph}^2} \frac{\partial^2 V}{\partial t^2}$$

$$V_{ph} = \sqrt{LC}$$

also $\frac{\partial^2 I}{\partial z^2} = \frac{1}{V_{ph}^2} \frac{\partial^2 I}{\partial t^2}$

There are solutions of the form

$$V(z, t) \sim Ae^{i(t-z/V_{ph})} + Be^{i(t+z/V_{ph})}$$

To find the current one uses one of the above equations;

$$\frac{\partial V}{\partial z} = -L \frac{\partial I}{\partial t}$$

$$\frac{i}{V_{ph}} \left(-A e^{i(t-z/V_{ph})} + B e^{i(t+z/V_{ph})} \right) = -L \frac{\partial I}{\partial t}$$

$$I(z, t) = \frac{1}{LV_{ph}} \left(-A e^{i(t-z/V_{ph})} + B e^{i(t+z/V_{ph})} \right)$$


So

$$I \sim \frac{V}{LV_{ph}} = \frac{V}{Z_0}$$

$$Z_0 = LV_{ph} = \sqrt{\frac{L}{C}}$$

The characteristic impedance.

For a coaxial line

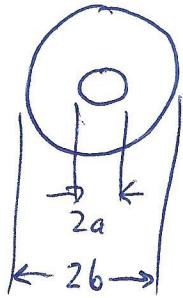

$$C = \frac{q}{\Phi_{0,ff}}$$

$$\Phi = - \int_a^b E_r dr = - \int_a^b \frac{q}{2\pi\epsilon r} = \frac{-q}{2\pi\epsilon} \ln(b/a)$$

$$C = \frac{2\pi\epsilon}{\ln(b/a)}$$

$$L = \frac{1}{I} \int_S \vec{B} \cdot d\vec{s}$$

$$\text{But } H_\phi = \frac{I}{2\pi r}$$

$$L = \frac{1}{I} \int_S \mu \frac{I}{2\pi r} dr dl = \frac{\mu}{2\pi} \int_a^b \frac{dr}{r} = \frac{\mu}{2\pi} \ln(b/a)$$

So far a coaxial cable;

$$V_{ph} = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\frac{\mu}{2\pi} \frac{1}{2\pi\epsilon} }} = \frac{1}{\sqrt{\mu\epsilon}} \quad \text{Same as free space!}$$

and

$$Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{\frac{\mu}{2\pi} \ln(6/a)}{\frac{2\pi\epsilon}{\ln(6/a)}}} = \sqrt{\frac{\mu}{\epsilon}} \frac{\ln(6/a)}{2\pi}$$

$$\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$$

$$\epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}$$

$$Z_0^{\text{Free Space}} = 376.8 \Omega$$

Antenna must match this.


$$Z_0^{\text{Coax}} = \sqrt{376.8 \Omega \frac{1}{\sqrt{2}} \frac{\ln(0.033/0.010)}{2\pi}}$$

$$= 50.6 \Omega$$

Universal Standard

Losses and Attenuation:

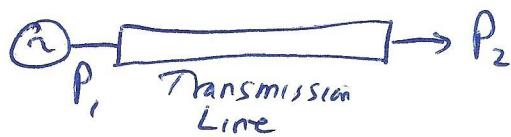Microwave Signals vary in magnitude over many orders, so it is convenient to use logarithms to discuss their losses.



$$\text{Loss (nepers)} = \frac{1}{2} \ln \frac{P_1}{P_2}$$

$$\text{Loss (dB)} = 8.686 \text{ Loss(nepers)}$$

$$\text{Loss (dB)} = 10 \log \frac{P_1}{P_2}$$

Suppose half of the power is lost in the transmission line

$$P_2 = P_1/2$$

$$\text{Loss (dB)} = 10 \log 2 = 3.01 \text{ dB}$$

3 dB is half power

Note that since $P \propto E^2$ or B^2

$$\text{Loss}_{E,B} (\text{dB}) = 20 \log \frac{E_1}{E_2}$$

The attenuation describes the loss in power per unit length. $\alpha \propto (\text{dB}/\text{length})$

$$\frac{P_2}{P_1} = 10^{-\frac{1}{10} \alpha \times \text{Length}}$$

$$\frac{V_2}{V_1} = \frac{I_2}{I_1} = 10^{-\frac{1}{20} \alpha \times \text{Length}}$$

For a normal metal transmission line $\alpha \propto \sqrt{f}$

For a superconducting transmission line $\alpha \propto f^2$

Dielectric Loss

$$Z_c = \frac{1}{i\omega\epsilon} \quad \sigma \sim i\omega C$$


$$\vec{J} = \sigma \vec{E}$$

$$\vec{J} = i\omega C \vec{E}$$

So the displacement current leads the voltage by 90° in an ideal lossless capacitor. If the dielectric is lossy, there is a real part of the conductivity, and there is a component of current in phase with the voltage

$$\vec{J} = (i\omega C + \sigma_{\text{real}}) \vec{E}$$
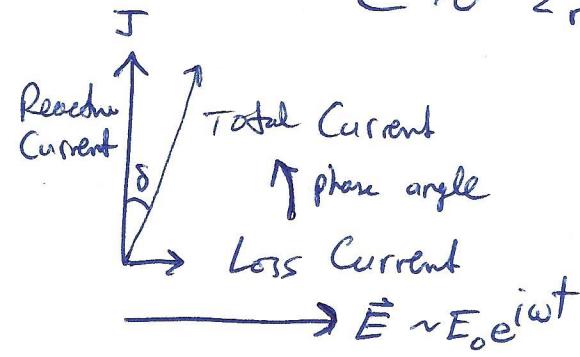
$$C \sim \epsilon_r \rightarrow \epsilon_r' + i\epsilon_r'' \quad \text{Complex Dielectric Constant}$$



$$\begin{aligned} \tan \delta &= \frac{\text{Loss Current}}{\text{Reactance Current}} \\ &= \epsilon_r'' / \epsilon_r' \end{aligned}$$

Attenuation in a dielectric is given by

$$\alpha_{\text{dielectric}} = \pi V_{ph} f \tan \delta \quad (\text{nepers/m})$$

$$\sim f^2$$


Standing Waves

Before we were talking about travelling waves. But in reality, we have waves travelling in both directions on the transmission line \rightarrow standing waves.

Any discontinuity in the uniform transmission line gives rise to standing waves.

In microwave circuits the concepts of voltage and current are meaningful only when a single mode is propagating.

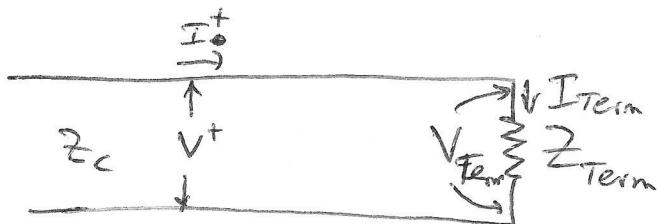Must establish a reference plane. The ratio of the voltage to current at that plane is defined as the device's impedance.



$$\frac{V^+}{I^+} = Z_c$$

For just one travelling wave going to the right.

$$\frac{V_{\text{Term}}}{I_{\text{Term}}} = Z_{\text{Term}}$$
 at the terminating impedance

The only way for $V^+ = V_{\text{Term}}$ and $I^+ = I_{\text{Term}}$ is if $Z_c = Z_{\text{Term}}$, that is the termination must have the same impedance as the coaxial cable.

If $Z_{\text{Term}} \neq Z_c$, then there must be a reflected wave. In that case

$$\frac{V^-}{I^-} = -Z_c$$

The total voltage and current are then

$$V = V^+ + V^-$$

$$I = I^+ + I^-$$

Require continuity at the terminating impedance

$$(V^+ + V^-)_{\text{at Term}} = V_{\text{Term}}$$

$$(I^+ + I^-)_{\text{at Term}} = I_{\text{Term}}$$

Combine these equations

$$V^+ + V^- = Z_{\text{Term}} I_{\text{Term}}$$

~~$$\frac{V^+}{I^+} - \frac{V^-}{I^-} = 2Z_c$$~~

~~$$V^+ - \frac{I^+}{Z_c} V^- = 2Z_c I^+$$~~

~~$$\frac{V^+}{I^+} + \frac{V^-}{I^-} = 0$$~~

$$\frac{I^+}{V^+} = \frac{1}{Z_c} \quad \frac{I^-}{V^-} = -\frac{1}{Z_c}$$

$$I^+ + I^- = \frac{1}{Z_c} (V^+ - V^-)$$

$$V^+ + V^- = Z_{\text{Term}} / Z_c (V^+ - V^-)$$

$$V^+ \left(1 - \frac{Z_T}{Z_C} \right) + V^- \left(1 + \frac{Z_T}{Z_C} \right) = 0$$

$$\boxed{V^- = V^+ \left(\frac{-1 + Z_T/Z_C}{1 + Z_T/Z_C} \right)}$$

(Ex)

Suppose $Z_{\text{Term}} = Z_C$, then

$$V^- = V^+ \left(\frac{-1+1}{1+1} \right) = 0$$

No reflection from a perfectly terminated line!

(Ex)

Suppose there is a short circuit at the load;
i.e. $Z_{\text{Term}} = 0$



Then

$$V^- = V^+ \left(\frac{-1}{1} \right) = -V^+$$


and all of the signal is reflected, with a 180° phase shift!

(Ex)

Suppose the transmission line ends with an "open" i.e. $Z_{\text{Term}} = \infty$, then

$$V^- = V^+ (1)$$

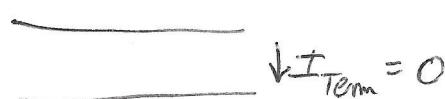This produces a complete reflection with no phase shift.



(Ex) Suppose the transmission line is left open to free space, $Z_{\text{load}} = 377 \Omega$

$$V^- = V^+ \left(\frac{377/50 - 1}{377/50 + 1} \right) = .76 V^+$$

$$P^- = .586 P^+$$

$\Gamma = .76$ reflection coeff

Reflection Coefficient: Ratio of the reflected to incident voltage

$$\Gamma = \frac{V^-}{V^+}$$

so that

$$\Gamma = \frac{Z_T/Z_c - 1}{Z_T/Z_c + 1} = |\Gamma| e^{j\theta}$$

θ is the angle by which the reflected voltage leads the incident voltage.

$$0 \leq |\Gamma| \leq 1$$

Return Loss

R compares the power in the reflected wave to the power in the forward wave

$$R(\text{dB}) = 10 \log_{10} \frac{\text{Incident Power}}{\text{Reflected Power}} = 10 \log_{10} \frac{|V^+|^2}{|V^-|^2} = 20 \log_{10} \frac{1}{|\Gamma|}$$

Totally reflecting termination $\rightarrow R = 0$

Totally absorbing termination $\rightarrow R \rightarrow \infty$

Transforming voltages on a transmission line

Suppose we know the voltage and current at w_1 , and we wish to calculate it at w_2 .

The forward voltage changes in magnitude $e^{\alpha(w_2-w_1)}$

The forward voltage changes in phase by $\beta(w_2-w_1)$


$$V^+(w_2) = V^+(w_1) e^{\alpha(w_2-w_1)} e^{i\beta(w_2-w_1)}$$

$$V^-(w_2) = V^-(w_1) e^{-\alpha(w_2-w_1)} e^{-i\beta(w_2-w_1)}$$

The reflection coefficient goes as

$$R(w_2) = R(w_1) e^{-2\alpha(w_2-w_1)} e^{-2\beta(w_2-w_1)}$$

Transformer Rule

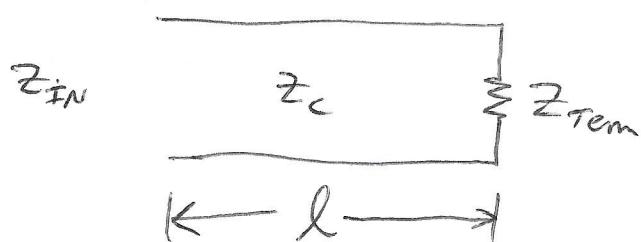

$$\bar{z}_{in} = \frac{\bar{z}_{Term} + i \tan \beta l}{1 + i \bar{z}_{Term} \tan \beta l} \quad \bar{z} = z/z_c$$

The transmission line of length l transforms the impedance of the termination to z_{in} .

Eamine the properties of various transmission lines

(Ex) Let $\bar{Z}_{\text{term}} = Z_c$, then $\bar{Z}_{\text{IN}} = 1$ or $Z_{\text{IN}} = Z_c$
for any length of line.

A perfectly terminated line has the impedance
of the transmission line

(Ex) Suppose $l = \lambda/2$ or $n\lambda/2$, then $\beta l = \pi$,
 $\tan \beta l = 0$ and

$$\bar{Z}_{\text{IN}} = \bar{Z}_{\text{term}}$$

so the transmission line is effectively "transparent"

Shorted and open transmission lines are practical
and have just about any impedance you want
(for a given λ).